

# Combinational network examples in VHDL

## Tutorial 04 on Dedicated systems

Teacher: Giuseppe Scollo

University of Catania  
Department of Mathematics and Computer Science  
Graduate Course in Computer Science, 2017-18

### Table of Contents

1. Combinational network examples in VHDL
2. tutorial outline
3. tri-state buffers
4. decoders
5. 7-segment display decoders
6. multiplexers
7. ALU functions
8. lab experience
9. RTL schematic of a 1-bit ALU
10. RTL schematic of a 3-bit ALU on FPGA
11. references

this tutorial deals with VHDL descriptions of frequently used hardware components:

- tri-state buffers
- decoders:
  - n-input decoders
  - 7-segment display decoders
- multiplexers
- ALU functions

various aspects and constructs of the VHDL language are introduced in the context of the proposed examples

furthermore, a lab experience is proposed which collects various aspects of VHDL that are illustrated by the examples presented here, and where some of these components may be reused for the implementation of the proposed experiment

### tri-state buffers

the standard, two-valued boolean type `BIT`, does not suffice to represent all situations that may come into play in circuit design

e.g. a circuit line may need be disconnected dynamically, in order to allow bus access by multiple drivers, one at a time

tri-state gates are typically utilized to this purpose


the IEEE 1164 standard defines the nine-valued `std_logic` type:

'U' Uninitialized  
'X' Forcing unknown  
'0' Forcing 0  
'1' Forcing 1  
'Z' High impedance  
'W' Weak unknown  
'L' Weak 0  
'H' Weak 1  
'-' Don't care

yet `std_logic` does not allow multiple driver access to the same line  
its subtype `std_logic` is endowed with a resolution function to resolve the contention, which is allowed thus

	U	X	0	1	Z	W	L	H	-
U	U	U	U	U	U	U	U	U	U
X	U	X	X	X	X	X	X	X	X
0	U	X	0	X	0	0	0	0	X
1	U	X	X	1	1	1	1	1	X
Z	U	X	0	1	Z	W	L	H	X
W	U	X	0	1	W	W	W	W	X
L	U	X	0	1	L	W	L	W	X
H	U	X	0	1	H	W	W	H	X
-	U	X	X	X	X	X	X	X	X

 contention resolution between values of type `std_logic`



```
library ieee;
use ieee.std_logic_1164.all;
entity tri_state is
  port (x, en : in std_logic;
        y : out std_logic);
end entity tri_state;
architecture when_else of tri_state is
begin
  y <= x when en = '1' else 'Z';
end architecture when_else;
```

## decoders

functional unit that proves useful to diverse purposes, for example:

memory chip/row selection

decoding of a machine instruction opcode

VHDL specification of the 2→4 decoder

```
library ieee;
use ieee.std_logic_1164.all;

entity decoder2 is
  port (
    a : in std_logic_vector(1 downto 0);
    z : out std_logic_vector(3 downto 0)
  );
end entity decoder2;


architecture when_else of decoder2 is
begin
  z <= "0001" when a = "00" else
    "0010" when a = "01" else
    "0100" when a = "10" else
    "1000" when a = "11" else
    "XXXX";
end architecture when_else;
```

generic VHDL specification of the decoder (Zwolinski, sect. 4.2.3):

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity decoder is
  generic (n : POSITIVE);
  port (
    a : in std_logic_vector(n-1 downto 0);
    z : out std_logic_vector(2**n-1 downto 0)
  );
end entity decoder;

 architecture rotate of decoder is
  constant z_out : BIT_VECTOR(2**n-1 downto 0) :=
    (0 => '1', others => '0');
begin
  z <= to_stdlogicvector(z_out sll
    to_integer(unsigned(a)));
end architecture rotate;
```



VHDL shift operators


## 7-segment display decoders

familiar device of daily use ...

a decoder for a seven-segment display converts a 4-bit input to the 7-bit configuration of the display segment states that visualizes the character corresponding to the (hex or decimal) digit which has the value coded by the input

the following example (taken from Zwolinski, Sect. 4.2.3)

 - visualizes decimal digits
- visualizes E if the input value is  $\geq 10$
- in all other cases the display is blanked



Zwolinski, Figure 4.3 - Seven-segment display

```
library ieee;
use ieee.std_logic_1164.all;

entity seven_seg is
  port (a : in std_logic_vector(3 downto 0);
    z : out std_logic_vector(6 downto 0));
end entity seven_seg;

architecture with_select of seven_seg is
begin
  with a select
    z <= "1110111" when "0000",
    "0010010" when "0001",
    "1011101" when "0010",
    "1011011" when "0011",
    "0111010" when "0100",
    "1101011" when "0101",
    "1101111" when "0110",
    "1010010" when "0111",
    "1111111" when "1000",
    "1111011" when "1001",
    "1101101" when "1010"|"1011"|"1100"|"1101"|"1110"|"1111",
    "0000000" when others;
end architecture with_select;
```


## multiplexers

VHDL description of a multiplexer with a single select input:

```
library ieee;
use ieee.std_logic_1164.all;
```

```
entity mux1 is
port (
    s : in std_logic;
    a : in std_logic;
    b : in std_logic;
    y : out std_logic
);
end entity mux1;
```
 
```
architecture basic of mux1 is
begin
    y <= a when s = '0' else
        b when s = '1' else
            'X';
end architecture basic;
```



how to generalize to  $n$ -select input?

description of an  $n$ -input OR gate:

```
library ieee;
use ieee.std_logic_1164.all;
entity wide_or is
generic (n : POSITIVE);
port (
    x : in std_logic_vector(n-1 downto 0);
    y : out std_logic);
end entity wide_or;
```

$n$ -select input multiplexer

```
library ieee;
use ieee.std_logic_1164.all;
entity mux is
generic (n : POSITIVE := 1);
port (
    s : in std_logic_vector(n-1 downto 0);
    a : in std_logic_vector(2**n-1 downto 0);
    z : out std_logic);
end entity mux;
```

instantiation of the generic multiplexer

```
library ieee;
use ieee.std_logic_1164.all;
entity mux2 is
port (
    s : in std_logic_vector(1 downto 0);
    a : in std_logic_vector(3 downto 0);
    z : out std_logic);
end entity mux2;
```

architecture sequential of wide\_or is

```
begin
    process (x) is
        variable z : std_logic;
    begin
        z := x(0);
        if n > 1 then
            for i in 1 to n-1 loop
                z := x(i) or z;
            end loop;
        end if;
        y <= z;
    end process;
end architecture sequential;
```

architecture structural of mux is

```
signal decout : std_logic_vector(2**n-1 downto 0);
signal andout : std_logic_vector(2**n-1 downto 0);
begin
    di: entity WORK.decoder generic map (n)
        port map (a => s, z => decout);
    oi: entity WORK.wide_or generic map (2**n)
        port map (x => andout, y => z);
    andout <= a and decout;
end architecture structural;
```

architecture instance of mux2 is

```
di: entity WORK.mux generic map (2)
    port map (s, a, z);
end architecture instance;
```

## ALU functions

an ALU is a multifunction unit: a control input selects the operation to be executed

an example of multifunction logic unit has the selection as specified in the table and may be described in VHDL as follows:

```
library ieee;
use ieee.std_logic_1164.all;
entity alu_logic is
generic (n : POSITIVE := 16);
port (
    a : in std_logic_vector((n-1) downto 0);
    b : in std_logic_vector((n-1) downto 0);
    s : in std_logic_vector(1 downto 0);
    q : out std_logic_vector((n-1) downto 0)
);
end entity alu_logic;
```

```
architecture with_select of alu_logic is
    constant undefined : std_logic_vector(n-1 downto 0) := (others => 'X');
begin
    with s select
        q <= a or b when "00",
            a and b when "01",
            not b when "10",
            a xor b when "11",
            undefined when others;
end architecture with_select;
```


S	function
00	$Q \leftarrow A \text{ or } B$
01	$Q \leftarrow A \text{ and } B$
10	$Q \leftarrow \text{not } B$
11	$Q \leftarrow A \text{ xor } B$

for operands wider than one bit, ALU's arithmetic function may be specified in either structural or functional style; the latter as follows

```
library ieee;
use IEEE.std_logic_1164.all;
entity adder is
generic(n-1 : POSITIVE := 16);
port (
    a : in std_logic_vector (n-1 downto 0);
    b : in std_logic_vector (n-1 downto 0);
    ci : in std_logic;
    sum : out std_logic_vector (n-1 downto 0);
    co : out std_logic
);
end entity adder;
```

architecture sequential of adder is

```
begin
    process(a,b,ci)
        variable carry : std_logic;
        variable psum : std_logic_vector(n-1 downto 0);
    begin
        carry := ci;
        for i in 0 to n-1 loop
            psum(i) := a(i) xor b(i) xor carry;
            carry := (a(i) and b(i)) or ((a(i) xor b(i)) and carry);
        end loop;
        sum <= psum;
        co <= carry;
    end process;
end architecture sequential;
```

 


the 8-bit ALU simulator implemented by S. Lentini and G. Nicotra illustrates how one can iteratively construct the 8-bit ALU by suitably composing 1-bit ALU stages

the schematic and an animated illustration of the ALU functions are presented in the "Arithmetic logic unit" part of the Flash animation of that project

using the VHDL constructs seen in the examples through this tutorial:

1. build a VHDL model of the 1-bit ALU; an equivalent solution to that which is represented by the schematic reproduced next, may be obtained by appropriate use of a multiplexer in place of a decoder
2. building on this result, construct a generic model of the  $n$ -bit ALU
3. compose a 3-bit instance of the generic ALU model with a VHDL model of the hex to 7-segment display decoder (available in the reserved lab area), mapping the I/O ports of the obtained model to pins of the DE1-SoC FPGA, as specified next and further illustrated in the subsequent RTL schematic
4. program the FPGA by using its 10 switches and 2 keys for the ALU input (the 2 keys for the ENA, ENB inputs, 6 switches for the A, B operands, the remaining switches for the other control inputs) and a 7-segment display for the visualization of the result (carry included, for addition)
5. test the functioning of the 3-bit ALU on the FPGA by acting on the switches and assigned keys


RTL schematic of a 1-bit ALU

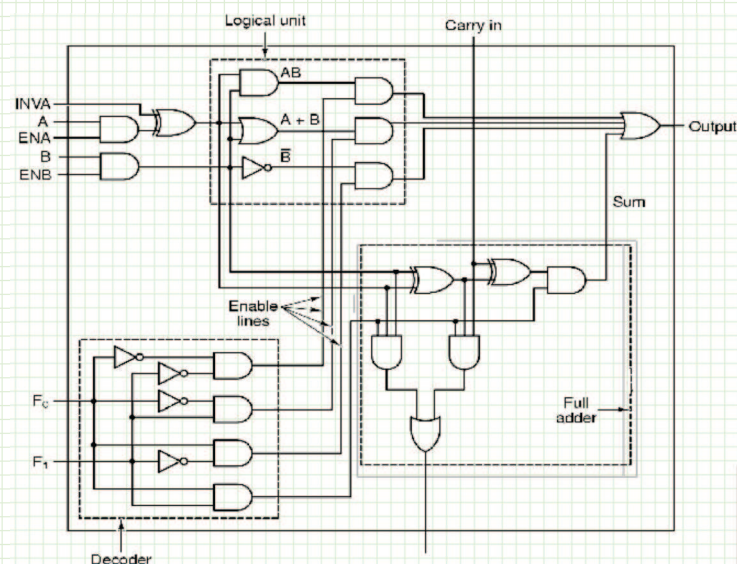

schematic of a 1-bit ALU (Figure 3-19 in (Tanenbaum, 2006))



RTL schematic of a 3-bit ALU on FPGA

 

RTL schematic of a 3-bit ALU generated by Quartus Prime Lite 16.1

## references

### recommended readings:

Zwolinski, Ch. 4, Sect. 4.1-6

### useful materials for the proposed lab experience

(sources: DMI Library, Altera University Program, 2016)

Tanenbaum: *Structured computer organization, Fifth Edition* (Pearson, 2006) Sect. 3.2.3

Making Qsys Components - For Quartus Prime 16.1, Appendix A

Quartus Prime Introduction Using VHDL Designs - For Quartus Prime 16.1, Sect. 9

DE1-SoC Quartus Setting File with Pin Assignments

### VHDL sources:

examples in this presentation

examples in Zwolinski book