

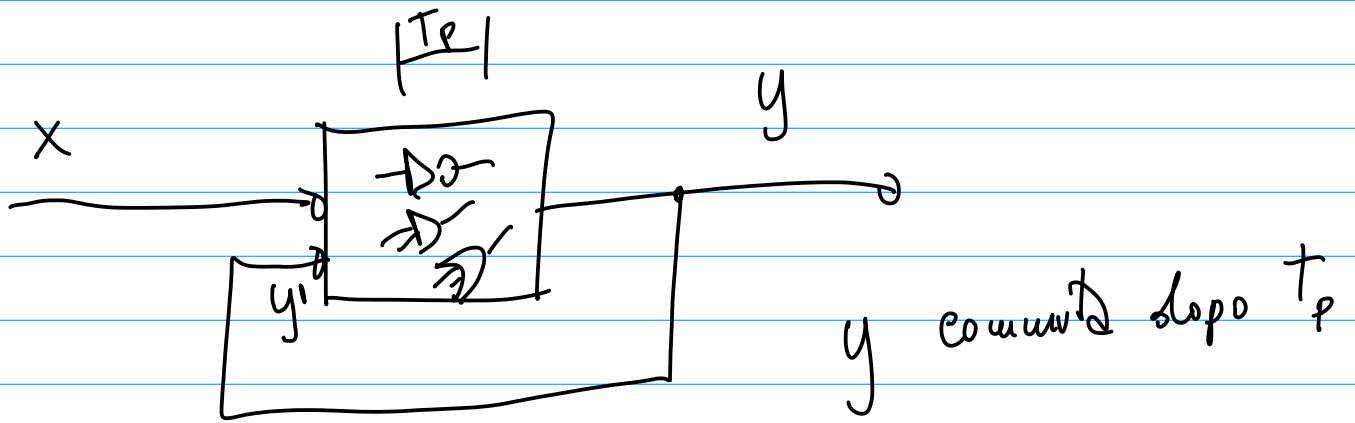


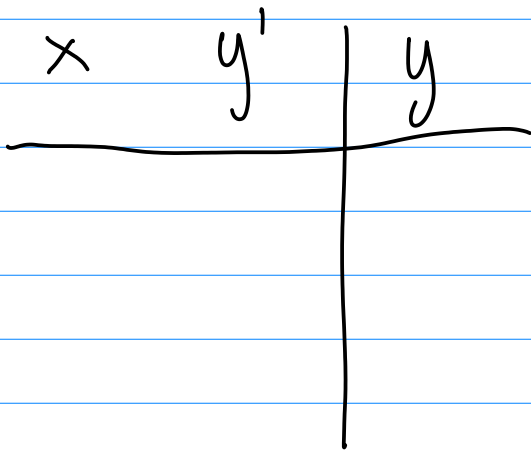

$y' \rightarrow$ passato $y' \rightarrow$ presente
 $y \rightarrow$ presente $y \rightarrow$ futuro

$y' =$ l'uscita al "tempo" precedente

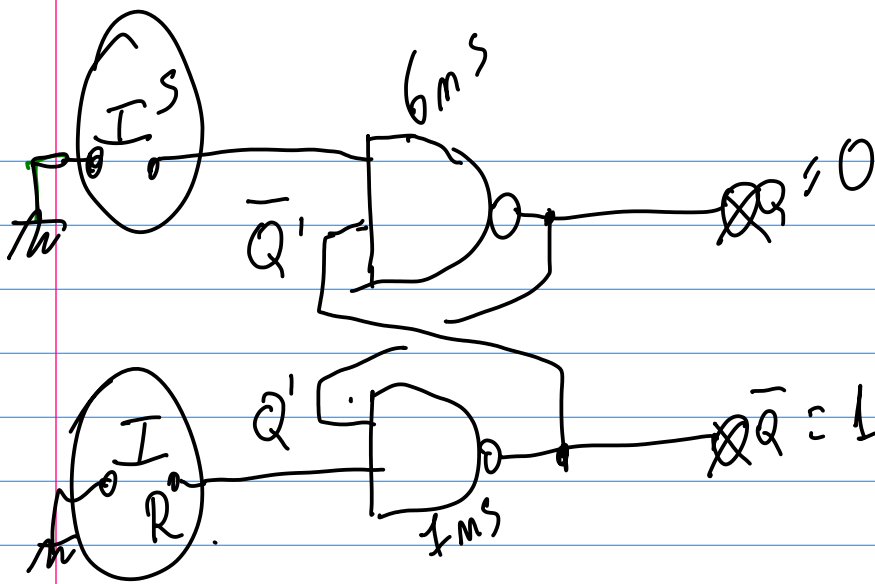



NAND

0	0	1
0	1	1
1	0	1
1	1	0

S	R	Q'	$\bar{Q}'$	Q	$\bar{Q}$
0	0	X	X	1	1
0	1	0	X	1	0
0	1	1	X	1	0
1	0	X	0	1	1
1	0	X	1	0	1
1	1	0	0	1	1
1	1	0	1	0	1
1	1	1	0	1	0
1	1	1	1	0	0

