
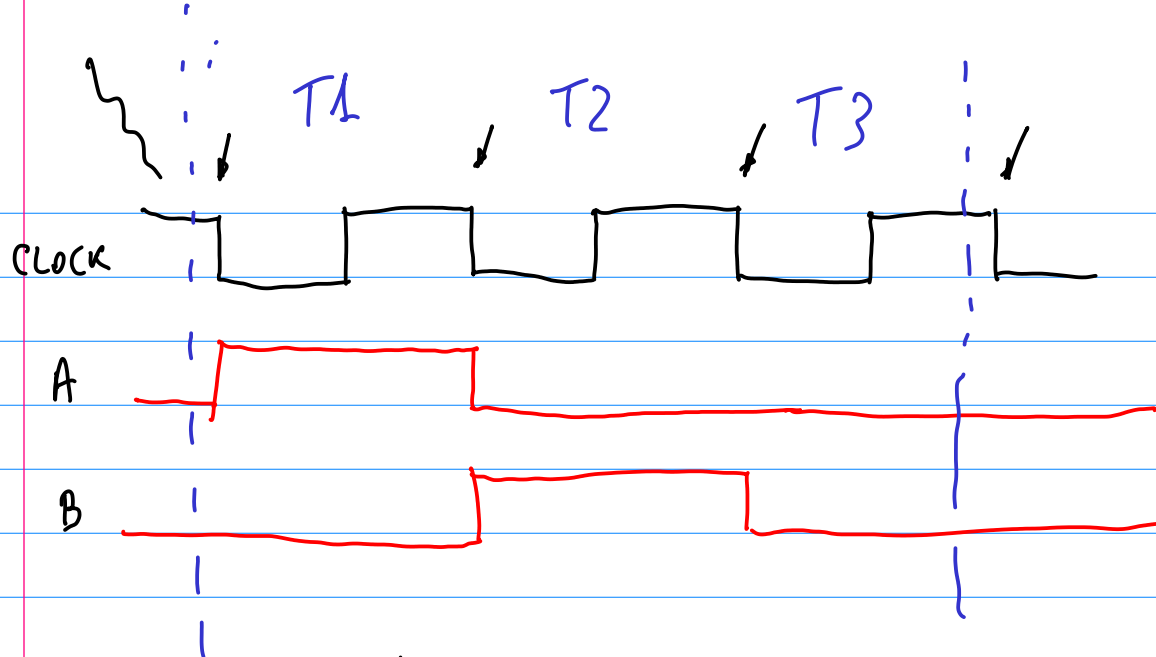


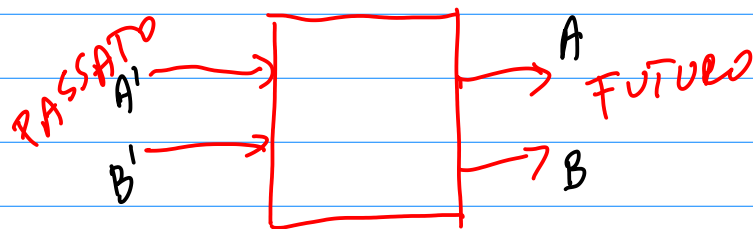

Clock	A	B
	0	0
T1	1	0
T2	0	1
T3	0	0



A'	B'	A	B
0	0	1	0
1	0	0	1
0	1	0	0

A'	B'	A
0	0	1
1	0	0
0	1	0

① $A = \overline{A'} \cdot \overline{B'}$

② $B = A' \cdot \overline{B'}$



A'	B'	B
0	0	0
1	0	1
0	1	0


$$\textcircled{1} \quad A = \widehat{A'} \cdot \overline{B'}$$

$$\textcircled{2} \quad B = A' \cdot \overline{B'}$$

PASSATO

FUTURO

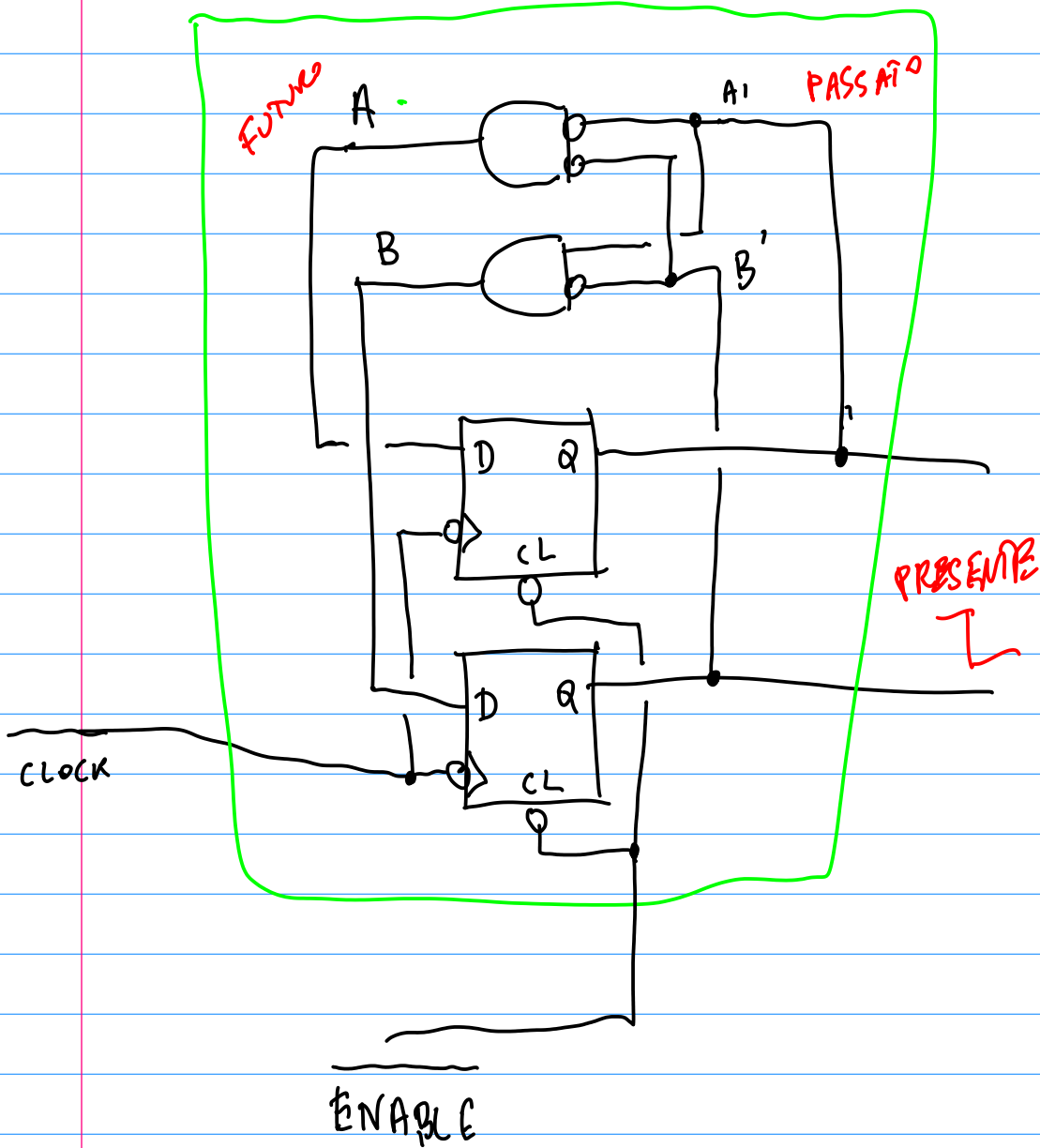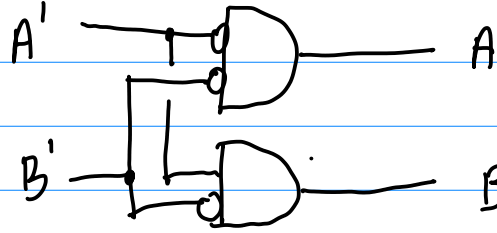

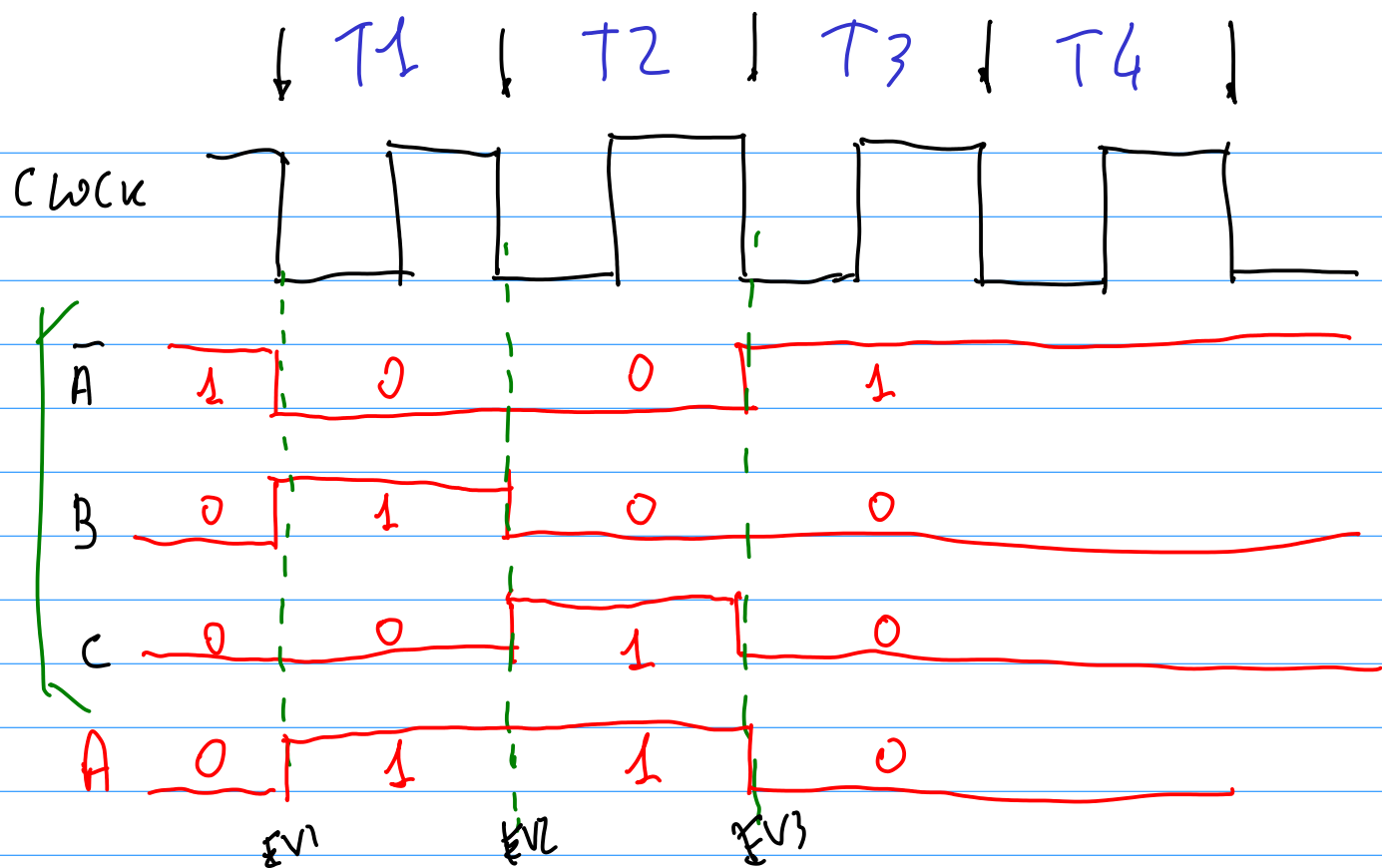


A'	B'	C'	A	B	C	
0	0	0	1	1	0	EV1
1	1	0	1	0	1	EV2
1	0	1	0	0	0	EV3

$$A = \bar{A}'\bar{B}'\bar{C}' + A'B'\bar{C}'$$

$$B = \bar{A}'\bar{B}'\bar{C}'$$

$$C = A'B'\bar{C}'$$

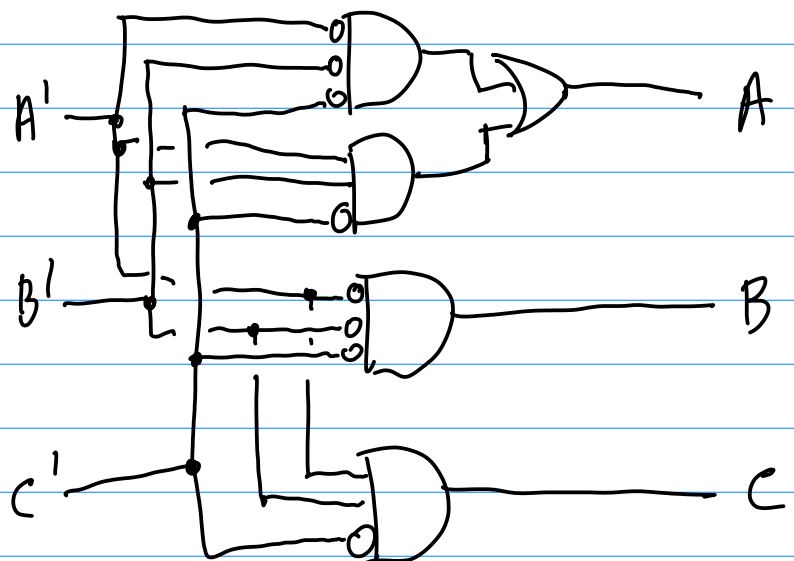

$$A = \bar{A}'\bar{B}'\bar{C}' + A'B'\bar{C}'$$

$$B = \bar{A}' \bar{B}' \bar{C}'$$

$$C = A'B' \tilde{C}^{-1}$$

