

Elements of Circuit Analysis

Corrado Santoro

ARSLAB - Autonomous and Robotic Systems Laboratory

Dipartimento di Matematica e Informatica - Università di Catania, Italy

santoro@dmi.unict.it



L.A.P. 1 Course




The Ohm's Law

The Kirchhoff Voltage Law (KVL)

The Kirchhoff Current Law (KCL)


Basic Elements of Direct Current (DC) Circuits

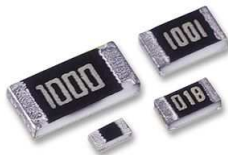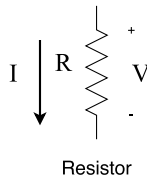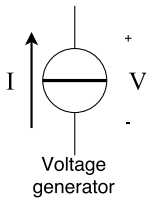- V , voltage (Volt), difference of electrical potential
- I , current (Ampere), flow of electrons in circuit components
- R , resistance (Ohm), ability to “oppose” to electron flow



The Ohm's Law

$$V = R I$$

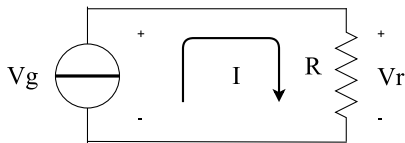


$$V_g = V_r$$
$$V_r = R I$$

The Ohm's Law

Given $V_g = 5V$ and $R = 10K\Omega$, calculate the current intensity

$$V = R I$$

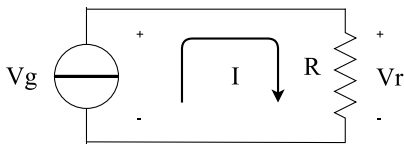


$$\begin{aligned} I &= \frac{V_g}{R} = \\ &= \frac{5}{10 \cdot 10^3} = \\ &= 0.5 \cdot 10^{-3} A = \\ &= 0.5 mA \end{aligned}$$

The Ohm's Law

Given $V_g = 5V$, calculate the resistance to obtain a current of $3A$


$$V = R I$$

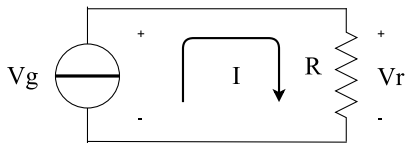

$$\begin{aligned} R &= \frac{V_g}{I} = \\ &= \frac{5}{3} = \\ &= 1.\bar{6}\Omega \end{aligned}$$

The Kirchhoff Voltage Law

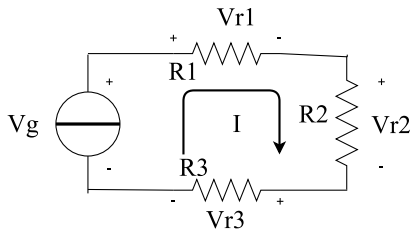The algebraic sum of the voltages in a circuit **loop** is equal to 0




$$-V_g + V_{R1} + V_{R2} + V_{R3} = 0$$

$$V_{R1} + V_{R2} + V_{R3} = V_g$$

The Kirchhoff Voltage Law

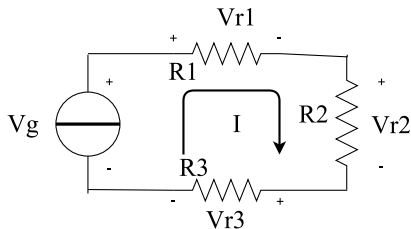Given $V_g = 5V$, $R1 = 220\Omega$, $R2 = 150\Omega$, $R3 = 18\Omega$, calculate V_{R1} , V_{R2} and V_{R3} .



$$V_g = V_{R1} + V_{R2} + V_{R3}$$


$$V_g = R1 I + R2 I + R3 I$$

$$V_g = (R1 + R2 + R3) I$$

$$I = \frac{V_g}{R1 + R2 + R3} = \frac{5}{220 + 150 + 18} = 0.013A$$

The Kirchhoff Voltage Law

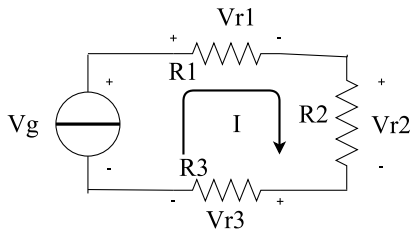Given $V_g = 5V$, $R1 = 220\Omega$, $R2 = 150\Omega$, $R3 = 18\Omega$, calculate V_{R1} , V_{R2} and V_{R3} .



$$I = \frac{V_g}{R1 + R2 + R3} = \frac{5}{220 + 150 + 18} = 0.013A$$


$$V_{R1} = R1 I = 220 \cdot 0.013 = 2.860V$$

$$V_{R2} = R2 I = 150 \cdot 0.013 = 1.950V$$

$$V_{R3} = R3 I = 18 \cdot 0.013 = 0.234V$$

The Kirchhoff Voltage Law

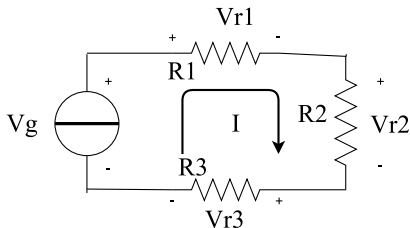Given the circuit below, calculate a generic formula that gives V_{R2} from V_g , $R1$, $R2$ and $R3$.



$$V_g = V_{R1} + V_{R2} + V_{R3}$$

$$V_g = R1 I + R2 I + R3 I$$


$$V_g = (R1 + R2 + R3) I$$

$$I = \frac{V_{R2}}{R2}$$

$$V_g = (R1 + R2 + R3) \frac{V_{R2}}{R2}$$

The Kirchhoff Voltage Law

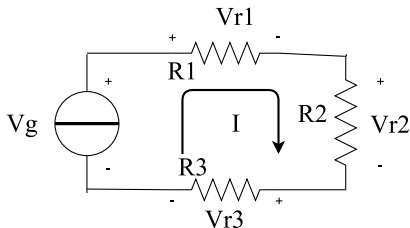Given the circuit below, calculate a generic formula that gives V_{R2} from V_g , $R1$, $R2$ and $R3$.




$$V_g = (R1 + R2 + R3) I$$

$$I = \frac{V_{R2}}{R2}$$

$$V_g = (R1 + R2 + R3) \frac{V_{R2}}{R2}$$

$$V_{R2} = \frac{R2}{R1 + R2 + R3} V_g$$


The Voltage Divider

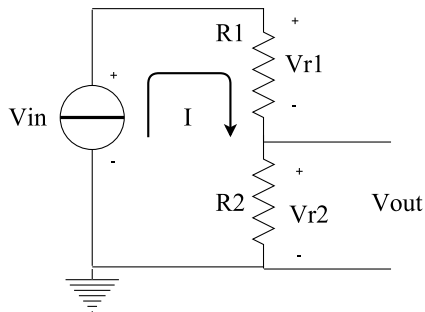

$$V_{out} = \frac{R_2}{R_1 + R_2} V_{in}$$

The Kirchhoff Current Law

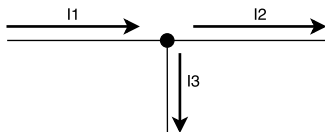The algebraic sum of the currents insisting in a circuit **node** is equal to 0




$$I_1 - I_2 - I_3 = 0$$

$$I_1 = I_2 + I_3$$

The Kirchhoff Voltage and Current Laws

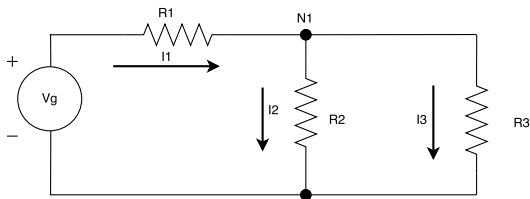Given $V_g = 5V$, $R1 = 220\Omega$, $R2 = 150\Omega$, $R3 = 18\Omega$, calculate all the currents and voltages on the resistors



$$V_g = V_{R1} + V_{R2}$$

$$V_{R2} = V_{R3}$$

$$I1 = I2 + I3$$


$$V_{R1} = R1 I1$$

$$V_{R2} = R2 I2$$

$$V_{R3} = R3 I3$$

The Kirchhoff Voltage and Current Laws

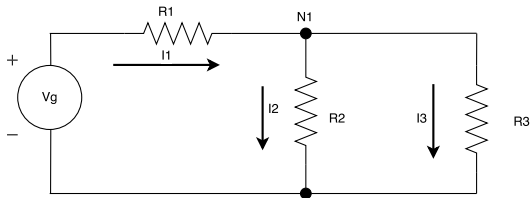
Given $V_g = 5V$, $R1 = 220\Omega$, $R2 = 150\Omega$, $R3 = 18\Omega$, calculate all the currents and voltages on the resistors



$$\left\{ \begin{array}{rcl}
 V_{R1} & + V_{R2} & = 5 \\
 & V_{R2} - V_{R3} & = 0 \\
 & & I_1 - I_2 - I_3 = 0 \\
 V_{R1} & & -220I_1 = 0 \\
 & V_{R2} & -150I_2 = 0 \\
 & & V_{R3} - 18I_3 = 0
 \end{array} \right.$$

The Kirchhoff Voltage and Current Laws

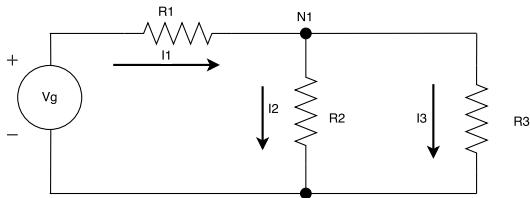Given $V_g = 5V$, $R_1 = 220\Omega$, $R_2 = 150\Omega$, $R_3 = 18\Omega$, calculate all the currents and voltages on the resistors



$$\left\{ \begin{array}{lcl} V_{R1} & = & 4.66V \\ V_{R2} & = & 0.35V \\ V_{R3} & = & 0.35V \\ I_1 & = & 21.2mA \\ I_2 & = & 2.3mA \\ I_3 & = & 18.9mA \end{array} \right.$$

Rules of Circuit Analysis



- 1 Apply Kirchhoff Voltage Law to loops
- 2 Apply Kirchhoff Current Law to nodes
- 3 Apply Ohm's Law to elements (resistors)
- 4 Derive n (linear) equation in n unknown variables
- 5 Solve the derived linear system

Semiconductors

Signal Diodes and Light Emitting Diodes (LEDs)


Diode

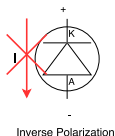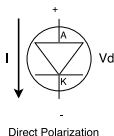- A **diode** is an electronic component made of “semi-conductor” materials (germanium, silicon, arsenic, gallium, ...)
- It has two wires **anode** and **cathode**
- If it is **directly polarized**, it causes a **voltage fall** of V_d (~0.7V in silicon diode, ~2.0V in LEDs) and permits current flow
- If it is **inversely polarized**, it impedes current flow



Analysis with Diode

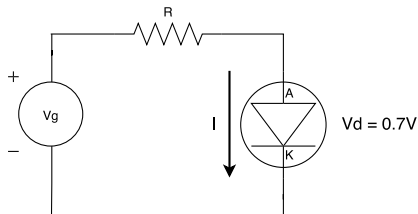Given $V_g = 5V$, $R = 220\Omega$, calculate the current I



$$V_g = V_R + V_d$$

$$5 = V_R + 0.7$$

$$V_R = 4.3$$


$$I = \frac{V_R}{R}$$

$$I = \frac{4.3}{220} = 0.02A = 20mA$$

How to compute the limiting resistor for a LED

- LEDs have a **forward voltage** of 1.2–3.0 V
- LEDs have a **forward current** that depends on the luminosity, in general in the order of 20 mA

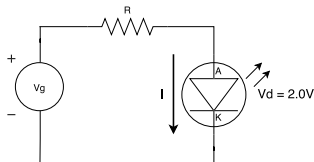Given $V_g = 5\text{ V}$ and $I = 20\text{ mA}$, compute the limiting resistance



$$V_g = V_R + V_d$$

$$5 = V_R + 2.0$$


$$V_R = 3$$

$$R = \frac{V_R}{I} = \frac{3}{0.02} = 150\Omega$$



Capacitors

Capacitors

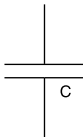- A **capacitor** is a circuit element able to **gather/store electric charge**
- It is composed of two **plates** separated by a **dielectric** (insulator)
- The electric energy is stored in plates and depends on the size and material of plates and insulator
- The **capacity** (ability to store electric energy) is measured in **Farad** (μF , nF , pF)





Dynamics of a capacitor

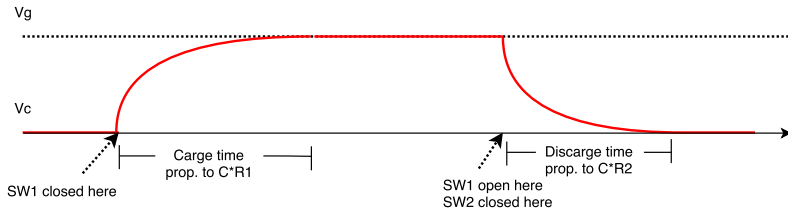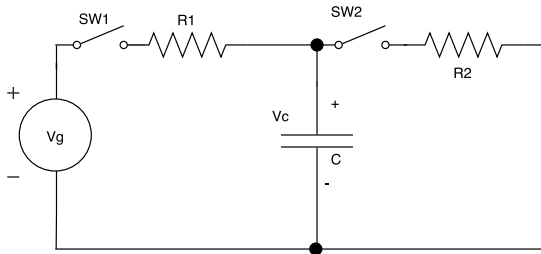

Capacitors as filters

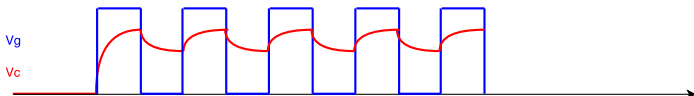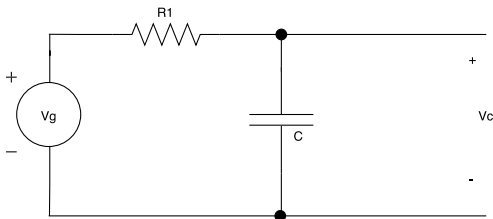- A capacitor with a resistor (**RC circuit**) act as a **filter**
- Here **V_g** is a generator of a **periodic signal** (a square wave)
- The RC circuit behaves by continuously charging and discharging the capacitor



Usage of Capacitors in digital circuits

- **By-pass capacitors:** placed between $V+$ and GND of a digital component, this capacitors are able to filter/remove spikes and other disturbances in the supply voltage
- **Debounce capacitors:** placed in parallel of push-buttons or switches are able to remove the “bouncing effect” of the mechanical parts

Elements of Circuit Analysis

Corrado Santoro

ARSLAB - Autonomous and Robotic Systems Laboratory

Dipartimento di Matematica e Informatica - Università di Catania, Italy

santoro@dmi.unict.it



L.A.P. 1 Course